
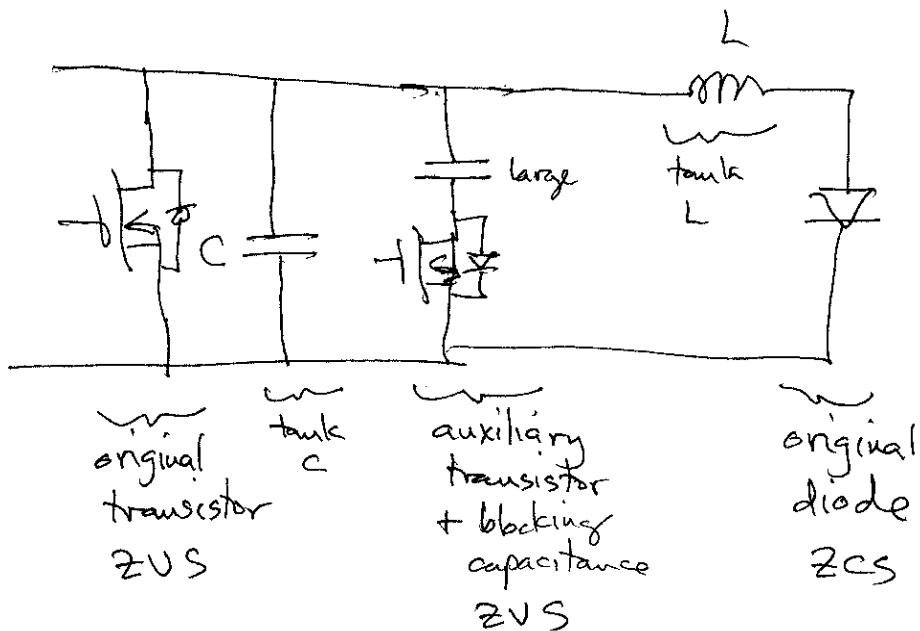


Active clamp snubber circuits

Basic version reduces to

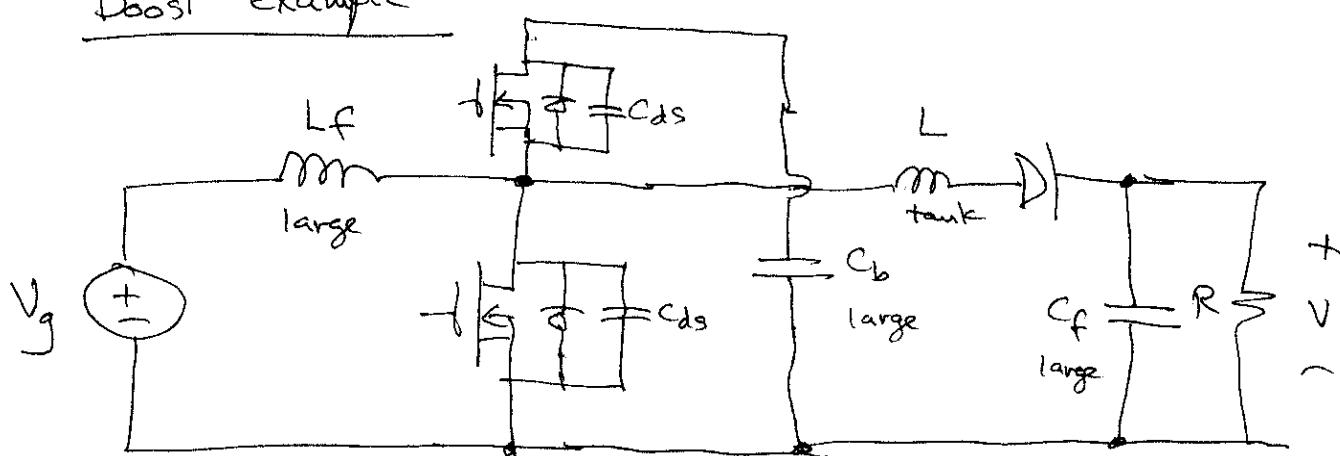


Boost example




This can be viewed as a resonant switch network that employs an auxiliary switch. The two MOSFETs form a half bridge circuit

2

Flyback example

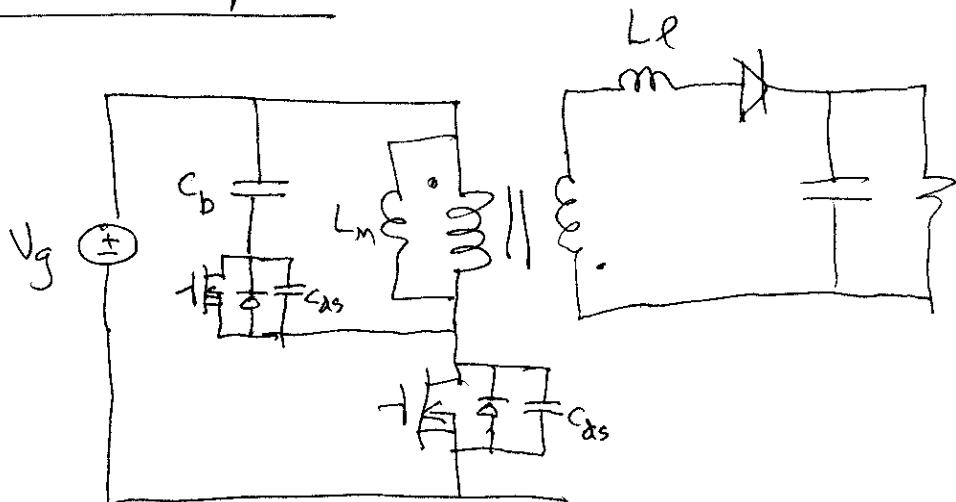

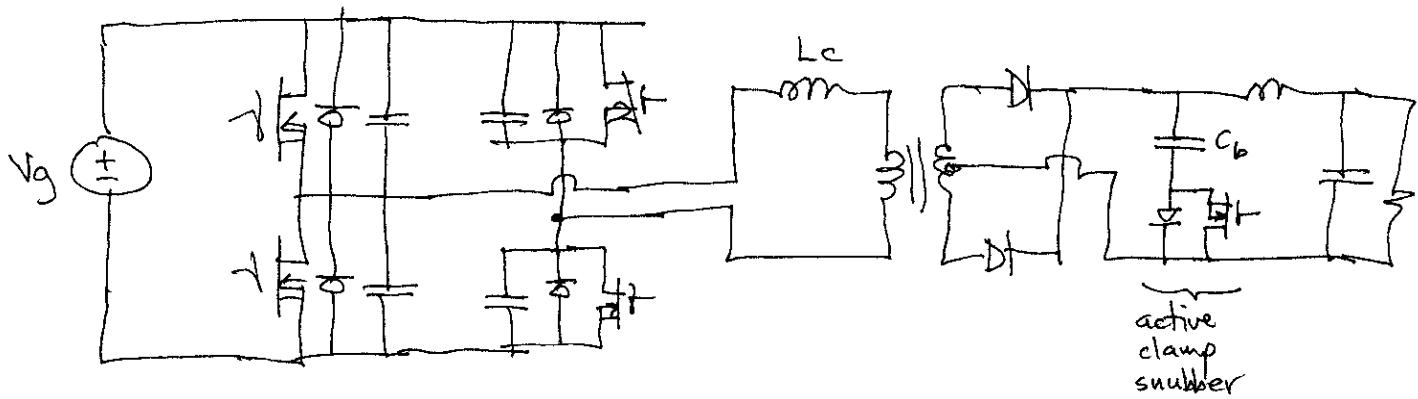ZVT bridge example - snubbing the output diodes




The above two applications can be viewed as improvements to the conventional dissipative voltage-clamp snubber




3

Forward converter version

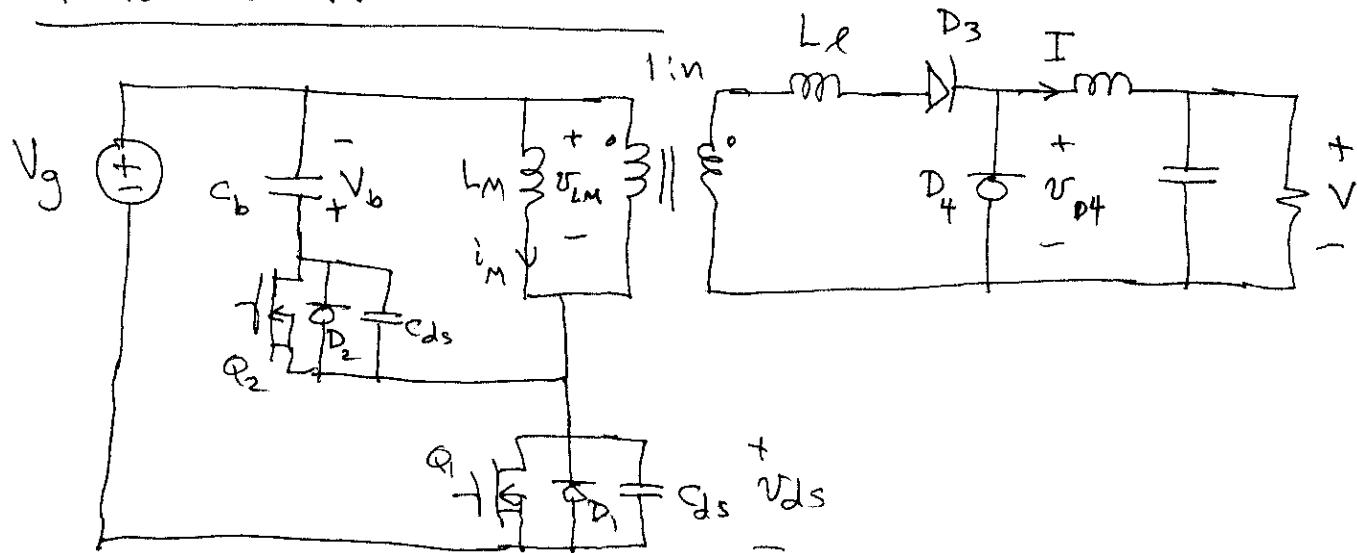

The auxiliary switch/active clamp circuit is used here to reset the transformer as well as to provide ZVS. The transformer is modeled with L_M , L_E , and ideal L-N transformer. MOSFET output capacitances C_{DS} participate in ZVS. For the analysis below, we will lump both C_{DS} into a single effective capacitance in parallel with Q_1 . Both L_M and L_E participate in operation of the tank.


(4)

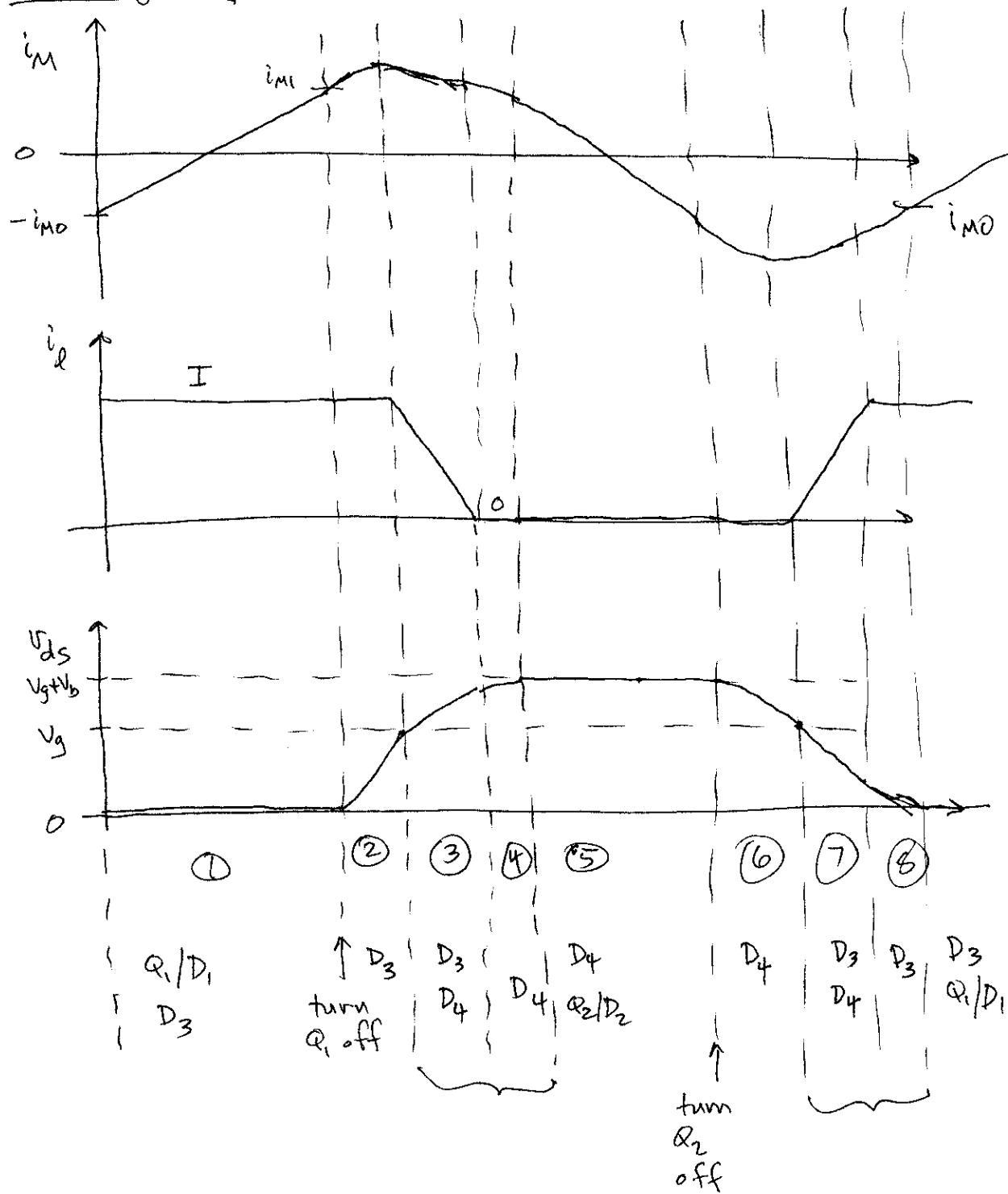Including L_L

Several details can be changed, which technically lead to different modes of operation. Interval ③ can end either when D_3 becomes reverse-biased by i_L reaching zero, or by D_2 becoming forward-biased when v_{DS} reaches $V_g + V_b$. In either event both happen by end of interval ④. Similar discussion (in reverse) applies to intervals ⑦ & ⑧.

(5)

Simplified waveforms—neglect L_e

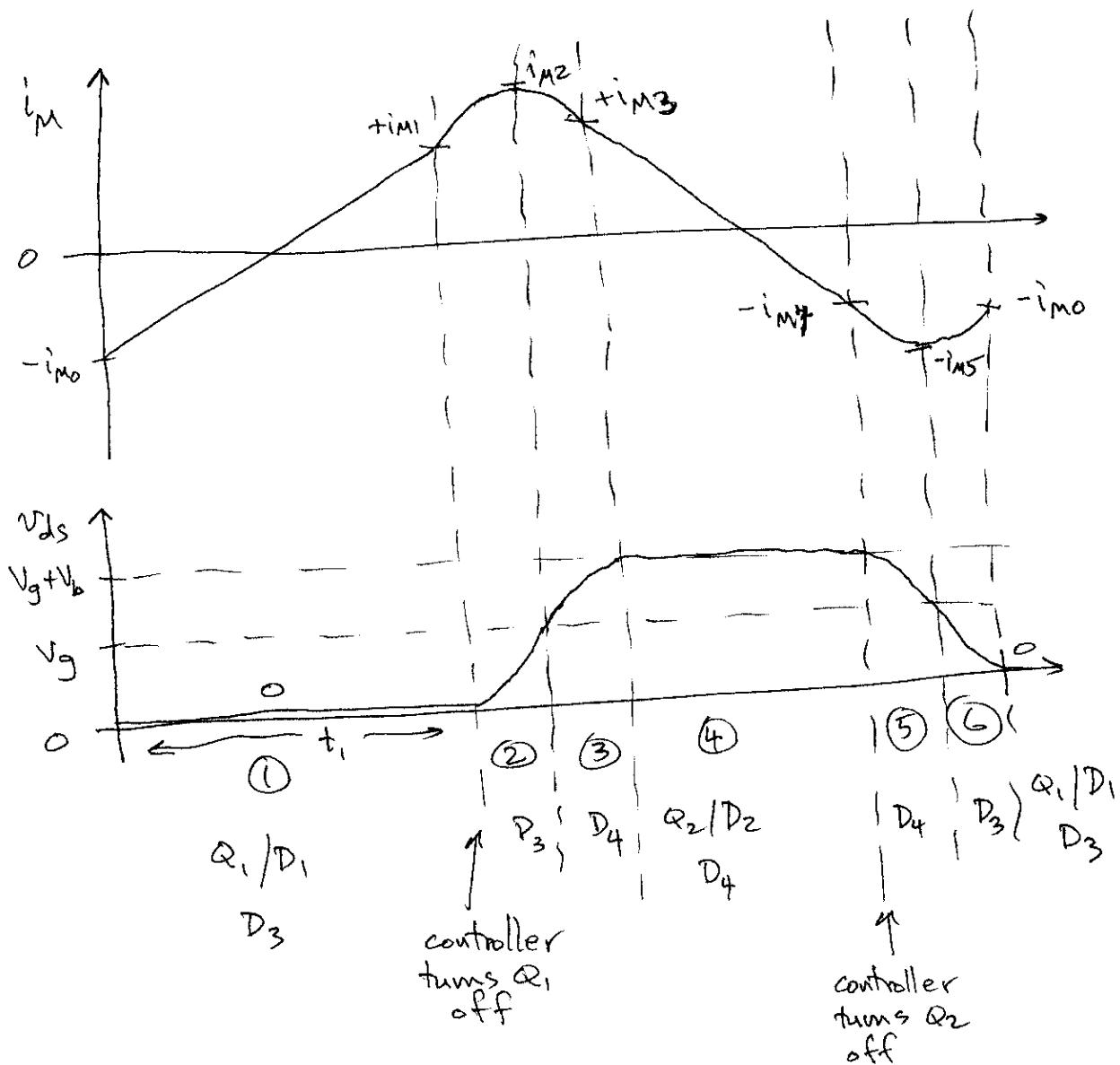

If we ignore L_e , then the model predicts that the load current I commutes instantly from D_2 to D_3 and vice-versa — secondary-side switching waveforms are idealized. But the primary-side switching behavior is modeled well. The predicted ZVS boundary is pessimistic.

(6)

Analysis

With L_e neglected, there is no multiresonant behavior. We can use the following base normalizing quantities for every subinterval:

$$V_{base} = V_g \quad I_{base} = \frac{V_g}{R_o} \quad R_o = \sqrt{\frac{L_M}{C_{ds}}}$$

$$\omega_0 = \frac{1}{\sqrt{L_M C_{ds}}}$$


where C_{ds} is the total capacitance seen at the drain of Q_1 (including the output capacitances of both Q_1 and Q_2)

$$\text{Define } J = \frac{uIR_o}{V_g} \rightarrow m_{ds} = V_{ds}/V_g \rightarrow j_m = i_M R_o / V_g$$

Subinterval ①

$Q_1/D_1, D_3$ conduct
interval ends when controller turns off Q_1

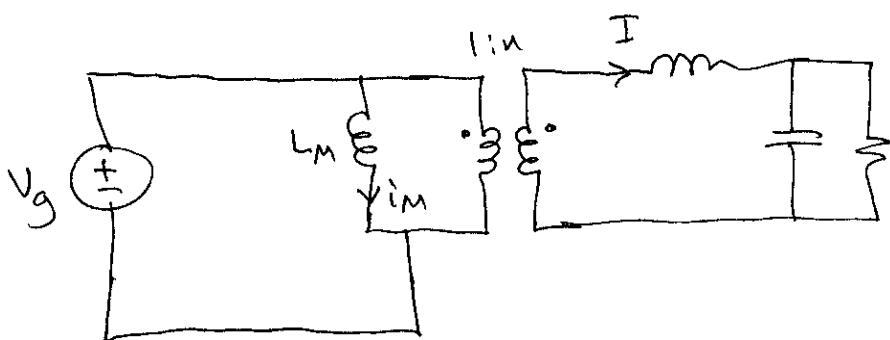
initial $j_m = -j_{m0}$, final $j_m = +j_{m1}$



$$\frac{di_m}{dt} = \frac{V_g}{L_M}, \quad i_{M1} = -i_{m0} + \frac{V_g t_1}{L_M} \Rightarrow t_1 = (i_{M1} + i_{m0}) \frac{L_M}{V_g}$$

$$\alpha = \omega_0 t_1 = j_{M1} + j_{m0}$$

(7)

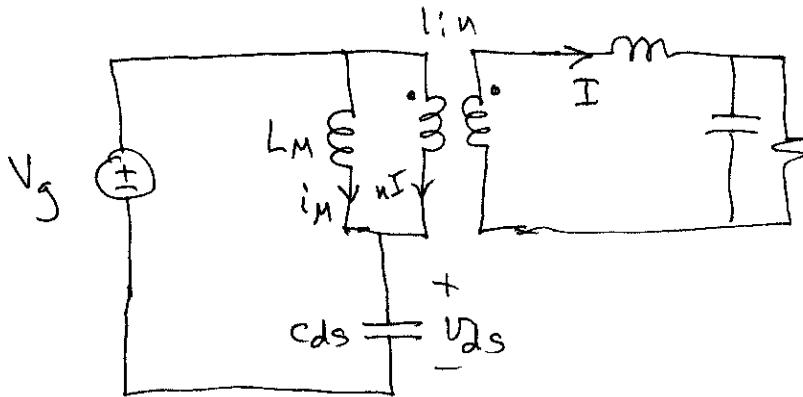
Subinterval ② D_3 conducts C_{ds} is charged by $i_M + uI$ interval ends when v_{ds} reaches V_g , causing the output diodes to switch

initial values:

$$v_{ds} = 0$$

$$i_M = i_{M1}$$

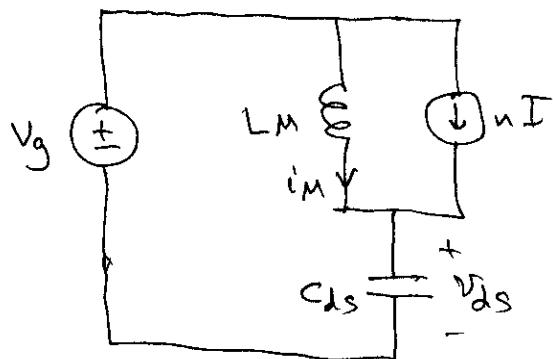Assume output filter inductor
is very large. Circuit
reduces to:




State plane trajectory
is circular, and is
centered at the
dc solution

$$v_{ds} = V_g, i_M = -uI$$

$$\Rightarrow v_{ds} = 1, j_M = -J$$

(8)

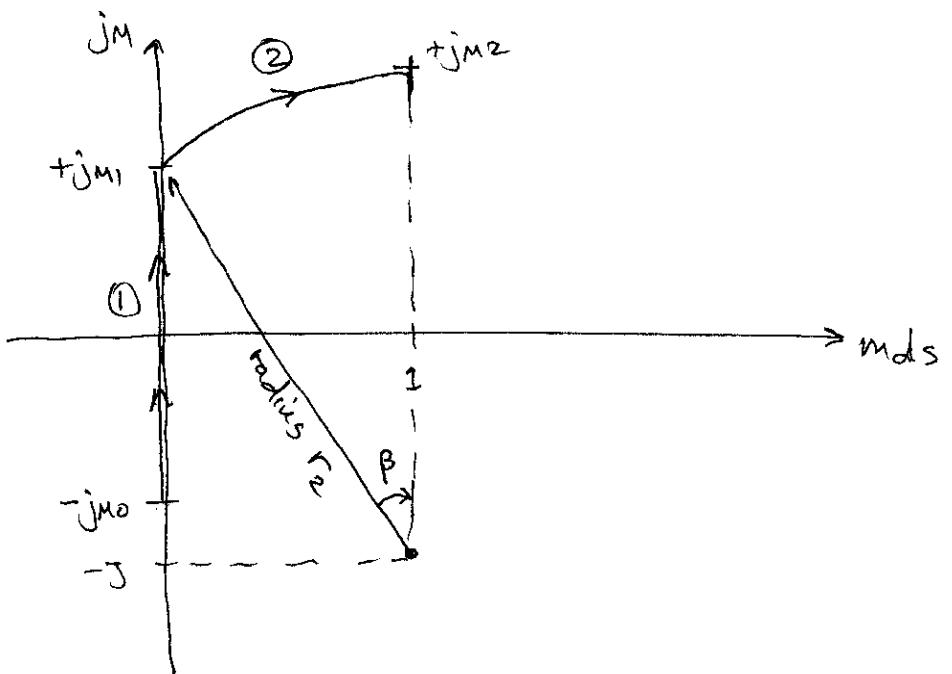

circle radius $r_2 = \sqrt{1 + (j_{M_1} + J)^2}$


final value $j_{M_2} = r_2 - J$

angle $\beta = \omega_0 t_2 = \tan^{-1}\left(\frac{1}{j_{M_1} + J}\right)$

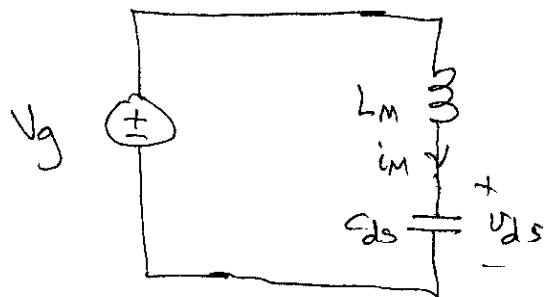(9)


Subinterval ③

D_4 conducts. We are ignoring the process by which the load current shifts from D_3 to D_4 — this commutation takes place during this subinterval.



initial $v_{ds} = V_g$, $i_m = i_{M2}$

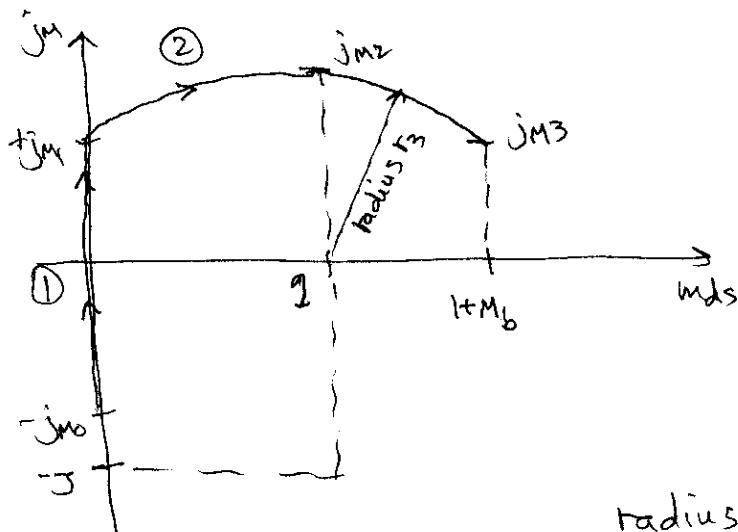interval ends when
 v_{ds} reaches $V_g + V_b$,
forward-biasing D_2



state plane
trajectory is
circle centered
at $j_m = 0$, $m_{ds} = 1$

$$\text{radius } r_3 = j_{M2}$$

At end of interval : $m_{ds} = 1 + M_b$ with $M_b = \frac{V_b}{V_g}$


final current : $j_{M3} = \sqrt{r_3^2 - M_b^2}$

For ZVS, require $r_3 > M_b$

interval length $\delta = \tan^{-1}\left(\frac{j_{M3}}{M_b}\right)$

(10)

Subinterval ④ Q_2/D_2 , D_4 conduct

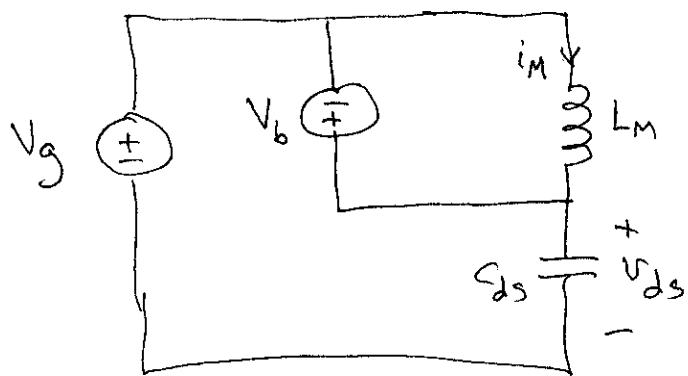

initial $i_M = i_{M3}$

$$\frac{di_M}{dt} = -\frac{V_b}{L_M}$$


interval ends when controller turns off Q_2

final current is $i_M = -i_{M4}$

$$-i_{M4} = i_{M3} - \frac{V_b}{L_M} t_4$$

$$-j_{M4} = j_{M3} - M_b \xi \quad \text{with } \xi = \omega_0 t_4$$

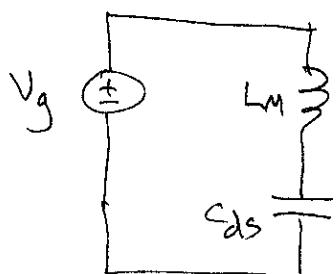Subinterval ⑤ D_4 conducts. interval ends when $v_{ds} = V_g$



initial $i_M = -i_{M4}$

$$v_{ds} = V_g + V_b$$


(see next page)

$$\text{circle radius } r_4 = \sqrt{M_b^2 + j_{M4}^2}$$

$$\text{final value } -j_{M5} = -r_4$$

$$\text{angle } \xi = \omega_0 t_5 = \tan^{-1}\left(\frac{M_b}{j_{M4}}\right)$$

(11)

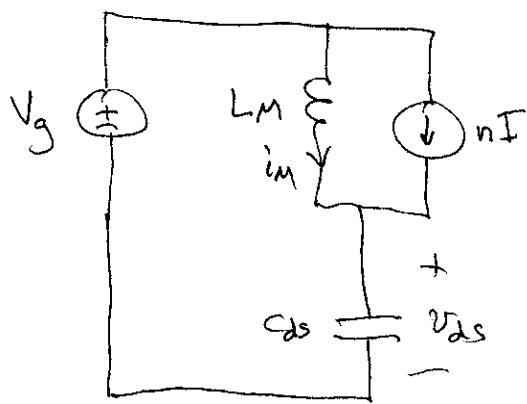Subinterval ⑥D₃ conducts, interval ends when
 $v_{ds} = 0$ 

Note magnetizing current i_m must oppose reflected load current nI to discharge C_{ds} .

Trajectory is circle centered at $j_m = -J$, $m_{ds} = 1$

$$\text{radius } r_5 = j_{M5} - J$$


final value:

$$-j_{M0} = -J - \sqrt{r_5^2 - 1}$$

For ZVS, require

$$r_5 \geq 1$$

$$\Rightarrow j_{M5} \geq 1+J$$

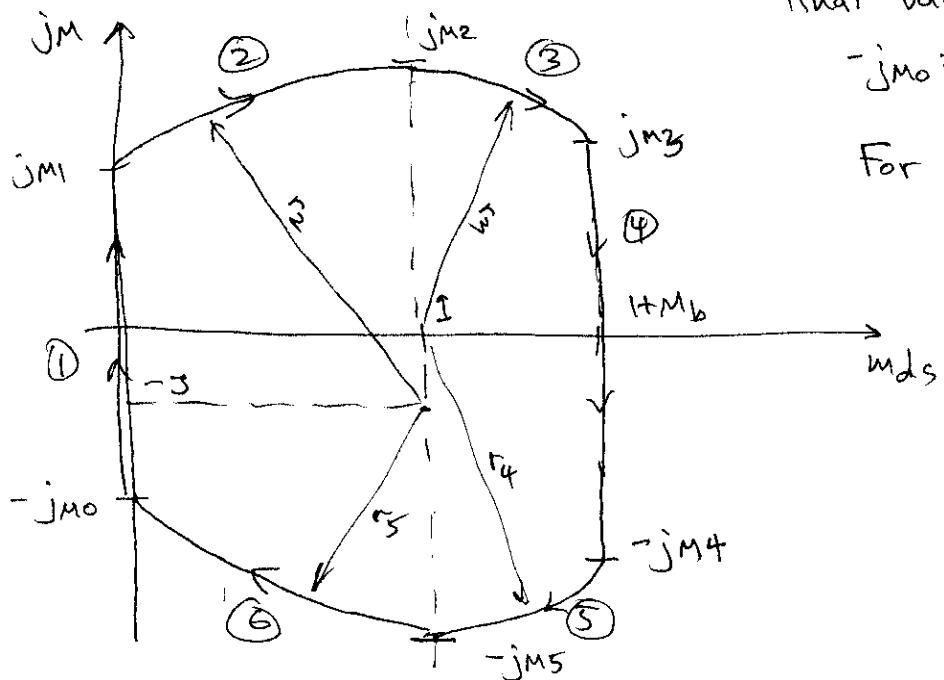


subinterval ⑥ length: $\psi = \omega_0 t_6 = \tan^{-1} \left(\frac{1}{j_{M0} - J} \right)$

Averaging

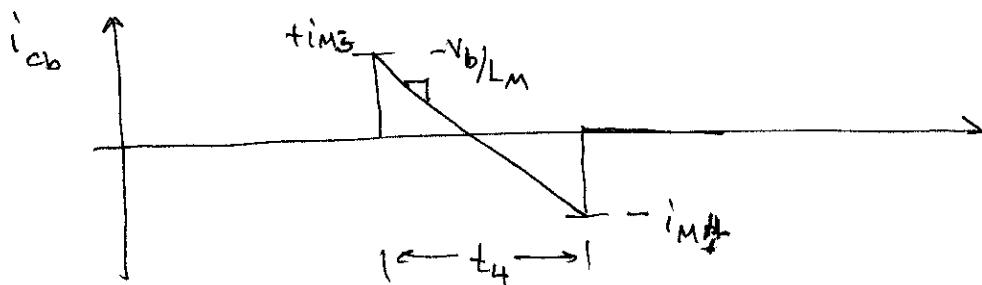A. charge balance on C_b


current flows through C_b only during subinterval ④, when Q_2/D_2 conduct:



For the net charge to be zero, we must have $i_{M3} = i_{M5}$. By symmetry of the state plane trajectory, this also implies that $i_{M2} = i_{M6}$

B. Volt-second balance on L_M

$$\tau_{LM} = v_{ds} - V_g$$

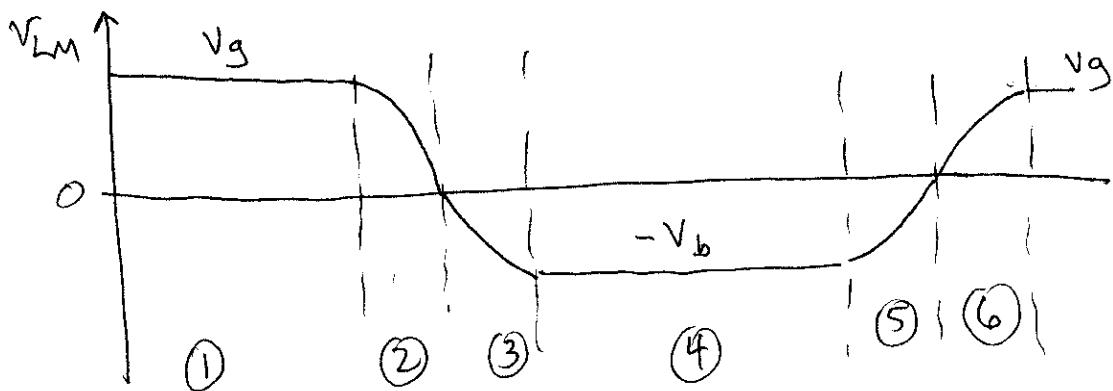

$$\langle v_{LM} \rangle = 0 \Rightarrow \langle v_{ds} \rangle = V_g$$

Note that volt-second balance is inherent in the state plane equations – if the state plane trajectory is closed, then the volt-seconds must balance.


(13)

C. Average output voltage

$$V = \langle v_{D4} \rangle$$

Note that $v_{D4} = 0$ while D_4 conducts - subintervals ③, ④, and ⑤. While D_3 conducts (subintervals ①, ②, and ⑥), $v_{D4}(t) = n v_{LM}(t)$. So
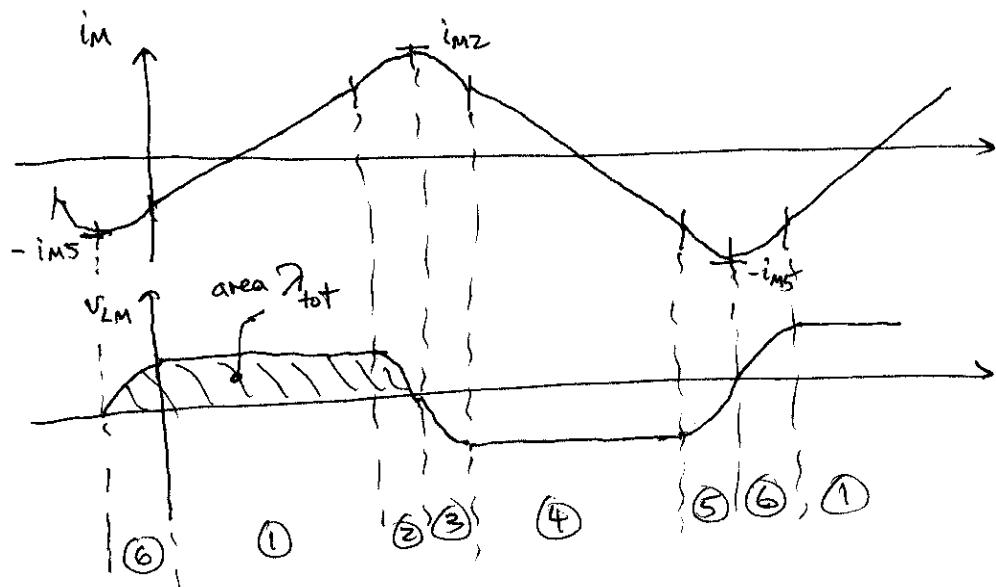
$$V = \frac{1}{T_S} \int_{\textcircled{1}, \textcircled{2}, \textcircled{6}} n v_{LM}(t) dt = \frac{n}{T_S} \lambda_{tot} \text{ with } \lambda_{tot} = \int_{\textcircled{1}, \textcircled{2}, \textcircled{6}} v_{LM}(t) dt$$



$$\text{Note } \lambda_{tot} = L_M (i_{M2} + i_{M5}) = 2L_M i_{M2}$$

$$\text{so } V = \frac{2nL_M i_{M2}}{T_S}$$

$$\text{and } M = \frac{V}{nV_g} = \frac{2L_M i_{M2}}{V_g T_S} = \frac{\cancel{2} \omega_0 L_M i_{M2}}{\cancel{V_g} \omega_0 T_S} = \frac{j_{M2} F}{\pi}$$

$\stackrel{= R_o}{\cancel{2}}$
 $\stackrel{= 2\pi/F}{\cancel{V_g}}$

$$\Rightarrow j_{M2} = \frac{M\pi}{F}$$

(14)

Summary of equations

$$\alpha = \omega_0 t_1 = j_{M1} + j_{Mo} \quad \text{subinterval } ①$$

$$j_{M2} = \sqrt{1 + (j_{M1} + J)^2} - J \quad \text{subinterval } ②$$

$$\beta = \omega_0 t_2 = \tan^{-1} \left(\frac{1}{j_{M1} + J} \right) \quad \text{subinterval } ③$$

$$j_{M3} = \sqrt{j_{M2}^2 - M_b^2}, \quad j_{M2} > M_b \quad \text{subinterval } ④$$

$$\delta = \omega_0 t_3 = \tan^{-1} \left(\frac{M_b}{j_{M3}} \right)$$

$$\xi = \omega_0 t_4 = \frac{j_{M3} + j_{M4}}{M_b} \quad \text{subinterval } ⑤$$

$$j_{M5} = \sqrt{M_b^2 + j_{M4}^2} \quad \text{subinterval } ⑥$$

$$\varsigma = \omega_0 t_5 = \tan^{-1} \left(\frac{M_b}{j_{M4}} \right)$$

$$j_{Mo} = J + \sqrt{(j_{M5} - J)^2 - 1}, \quad j_{M5} \geq 1 + J \quad \text{subinterval } ⑦$$

$$\chi = \omega_0 t_6 = \tan^{-1} \left(\frac{1}{j_{Mo} - J} \right)$$

$$j_{M3} = j_{M4}; \quad j_{M2} = j_{M5} = M\pi/F \quad \text{results of averaging}$$

$$\omega_0 T_S = \frac{2\pi}{F} = \alpha + \beta + \delta + \xi + \varsigma + \chi \quad \text{switching period}$$

$$\omega_0 DT_S = \varsigma + \chi + \alpha = \omega_0(t_5 + t_6 + t_1) \quad \text{duty cycle definition}$$

(15)

Solution requires computer iteration

Approximate results:

$M \approx D$		output voltage
$M_b \approx \frac{D}{1-D}$		clamp capacitor voltage
$\frac{M\pi}{F} \geq 1+J$		ZVS boundary

"Exact" solution for M_b :

$$M_b = \frac{M\pi}{F} \cdot \sin \left[\omega_0 DT_s - \sqrt{\left(\frac{M\pi}{F} + J\right)^2 - 1} + \sqrt{\left(\frac{M\pi}{F} - J\right)^2 - 1} \right. \\ \left. + \sin^{-1} \left(\frac{1}{\left(\frac{M\pi}{F} - J\right)^2} \right) \right]$$

Peak magnetizing current is $j_{M2} = \frac{M\pi}{F}$